



**North South University**  
Department of Electrical & Computer Engineering

**LAB REPORT**

Course Code: EEE 141

Course Title:

Faculty: RQN

Experiment Number: 3

Experiment Name:

Loading Effect of Voltage Divider Circuit

Experiment Date:

Date of Submission: 5/3/25

Section: 19

Group Number:

Submitted To: KASHFIA MAHMOOD

Submitted By:			Score
Serial No	Student Name	ID	
	K M Ahsan Orab	2222630042	
02	Nadim Mahmud	1921877642	
10	Dilshad Karim	2223014042	

## Experiment NAME: Loading Effect of Voltage and Divider Circuit

### Objectives:

1. To analyze how the voltage divider circuit behaves when there is no load resistance connected.
2. Evaluate the performance of the voltage divider circuit due to loading

### Apparatus:

1. Trainer Board
2. DMM
3.  $2 \times 560 \Omega$  resistors
4.  $1 \times (0-10k\Omega)$  variable resistor

### Theory:

Voltage divider Rule: The voltage rule is the voltage is divided between two series resistors in direct proportion to their resistance.


Loading Effect: When an instrument of lower sensitivity is used with a load the measurement it makes is erroneous, this effect is known as the loading effect.

Potentiometer: A potentiometer is a three-terminal resistor with a sliding or rotating contact that forms an adjustable voltage divider. If only two terminals are used, one end and the wiper, it acts as a variable resistor.


Application of Potentiometer: Potentiometers are used to directly control significant amounts of power. Instead, they are used to adjust the level of analog signals (for example Volume controls on audio equipment), and as control inputs for electronic circuits. For example, a light dimmer ~~uses~~ uses a potentiometer to control the switching of a TRIAC and so indirectly to control the brightness of lamps.

The reason we connect load at the end of the circuit: When we observed from the source end, the word end means the end of the circuit. The output end is where the circuit is designed to deliver power, and the output is where the load is to be utilized. In our home, the power outlets are the output end and the local distribution transformation is the input end. We connect them at the end because of:

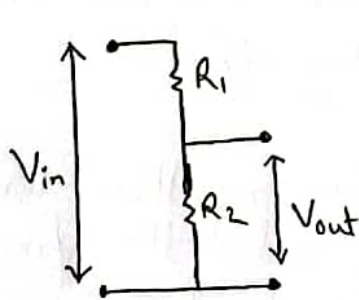1. A heavy load will draw more current while a light load will draw less current.
2. In the case of load less circuit, it will draw minimal current.




Voltage Divider

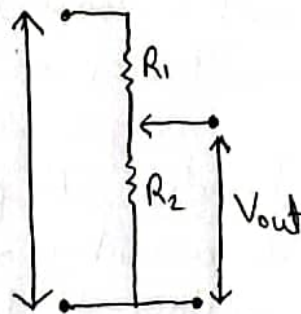



### Circuit Diagram:

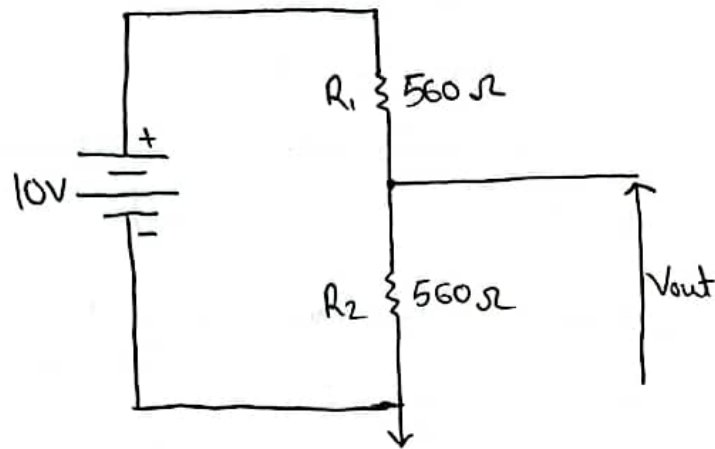

### # Result and Analysis:

In this experiment, we get to know about the effects of load resistance. If we want to add a potentiometer which is a variable resistance. We set it on parallel with  $R_2$ . We have to be very careful about connecting. We can connect with leg-A, B or B, C. We cannot connect leg A, C.


Here, we have three resistors and a variable resistor. 1<sup>st</sup> Zones are connected in series. We have to find each voltage and current for every resistance. For 1<sup>st</sup> measurement, there is no load resistance and now we got the highest voltage output. For the 2<sup>nd</sup> measurement, we add  $40\Omega$  load resistance. And now  $V_{out}$  drops. But as we increase load resistance also rises.

We did their careful measurement of all values. We observed the voltage divider circuit in this experiment we have learned how to create a ladder circuit, how to form a voltage

voltage divider circuit on a breadboard and we knew the use of variable resistors. For this experiment, the variable resistor was very sensitive for us, actually its measurement. There were very small differences between the theoretical and experimental values such differences can be avoided.

No problem was faced while doing the experiment. But one thing, because of some issues in the components, the theoretical and practical values were slightly different.


In conclusion, we have learned about the loading effect of the voltage divider circuit. We have learned about ladder circuits also, with a variable resistor. We can build the voltage divider circuit. We measured all values including practical and theoretical values. While doing the lab we tuned the variable resistor to get our actual need. Without some DMM and other components issues, the lab was knowledgeable and comfortable for our learning.

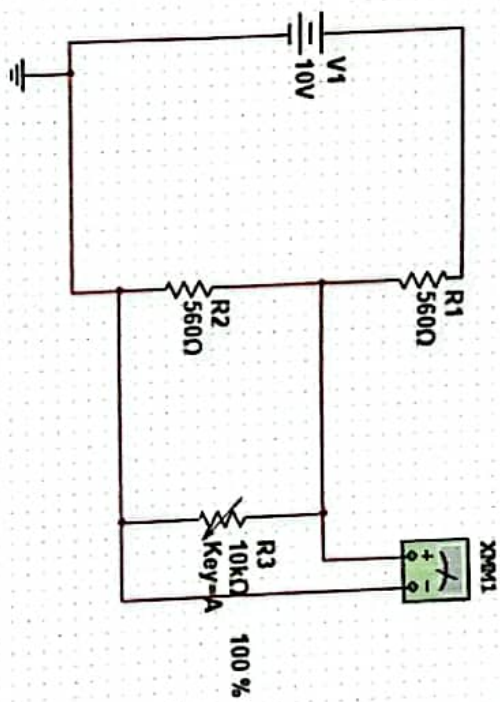

K M Ahsan Orab  
 2222630042





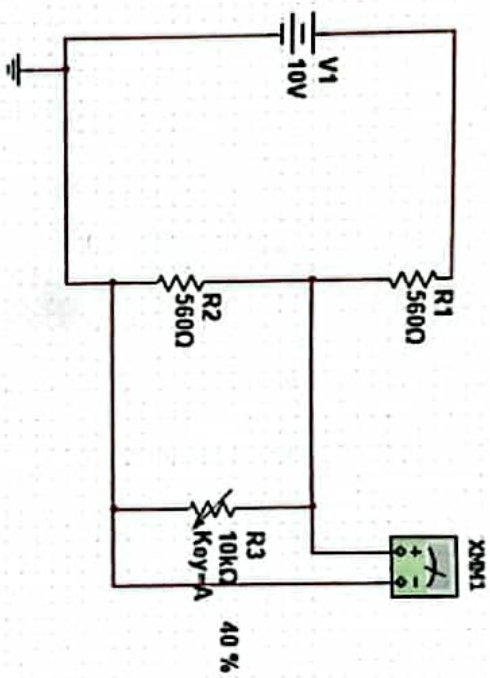

K M Ahsan Orab  
2222630042



## Questions:

1. Loading refers to the phenomena that occur when a load circuit having low effective impedance is connected to a supply circuit having a higher impedance. So on connecting the load circuit effectively reduces the resistance, drawing more (load) current causing greater voltage drop in the supply circuit. Consider a lower sensitivity (ohm per volt) voltmeter being used with a high resistance load. Now, as we may know a voltmeter is connected in parallel with the load, such a (low sensitivity) voltmeter when connected across a high resistance load forms a low resistance parallel path for current to pass through thus lowering the overall resistance of the arrangement and thus lowering the voltage drop across it, this causes erroneous readings by the voltmeter.

$$2. V_{out} (\text{No resistor}) = 10 \left( \frac{0.56/1}{0.56(0.56/1)} \right) \\ = 5V$$

$$V_{out} (1k) = 10 \left( \frac{\frac{0.56 \times 1}{0.56 + 1}}{0.56 \left( \frac{0.56 \times 1}{0.56 + 1} \right)} \right) \\ \approx 3.9V$$

$$V_{out} = 10 \left( \frac{\frac{0.56 \times 4}{0.56 + 4}}{0.56 \left( \frac{0.56 \times 4}{0.56 + 4} \right)} \right) \\ \approx 4.67V$$



$$V_{out}(7k) = 10 \frac{0.56 \left( \frac{0.56 \times 7}{0.56 + 7} \right)}{0.56 + \left( \frac{0.56 \times 7}{0.56 + 7} \right)}$$

$$= 4.8V$$

$$V_{out} = 10 \frac{0.56 \left( \frac{0.56 \times 10}{0.56 + 10} \right)}{0.56 + \left( \frac{0.56 \times 10}{0.56 + 10} \right)}$$

$$= 4.86V (A_{\sim})$$

3. Comparing the data we measured and calculated there's a slight error. The relatively accurate to the calculated readings prove that our experiment was a success. The difference in values must be for the shift in variable resistor while handling.

# NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



EEE41L/ETE141L

## Data Collection for Lab 3:

Group No. \_\_\_\_\_ Instructor's Signature \_\_\_\_\_

Table 1:

RL	Vout (Measured)	Vout (Calculated)	%Error
No resistor	4.95	5	1
1k	3.89	3.90	0.25
4k	4.65	4.67	0.43
7k	4.77	4.80	3.125
10k	4.82	4.86	3.6

## Report Question:

1. Explain the loading effect of your circuit (i.e explain how does your Vout vary with increasing Load resistor)
2. Showing all steps in details, theoretically calculate the value of Vout for each load resistor.
3. Comparing the theoretical data to the experimental data, comment how far the loading effect of your circuit supports the theory.