



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Code: FEE-141L

Course Title: Electrical circuits Lab

Faculty: RQN

Experiment Number: 2

Experiment Name:

KCL, Current divider rule with parallel and ladder circuit

Experiment Date: 14-02-25

Date of Submission: 26-02-25

Section: 19

Group Number: 02

Submitted To: KASHFIA MAHMOOD

Submitted By:			Score
Serial No	Student Name	ID	
02	Nadim Mahmud	1921877642	
10	Dilshad Karim	2223014042	
08	K M Ahsan Otab	2222630042	

1. Experiment name: KCL, Current Divider Rule with parallel and ladder circuit.

2. Objectives:

- * Learn how to connect parallel circuit on breadboard.
- * Validate the current divider rules and verify KCL and KVL in ladder circuit.

3. Apparatus:

- * Trainer board
- * Resistors ($1k$, $3.3k\Omega$, $4.7k\Omega$, $5.6k\Omega$, $10k\Omega$)
- * Digital Multimeter (DMM)
- * Connecting wire.

4. Theory:


The current divider rule is a key concept in electrical circuits. It is used to calculate how current is shared between the parallel branches of a circuit. It is based on Ohm's Law.

The voltage across each branch remains constant, but the current in each branch can differ.

The current divider rule states that the electrical current entering the node in a parallel circuit is divided into the branches. The current divider rule is used to calculate the magnitude of divided current in circuits.

A parallel circuit and a voltage source is shown below.

A parallel circuit:

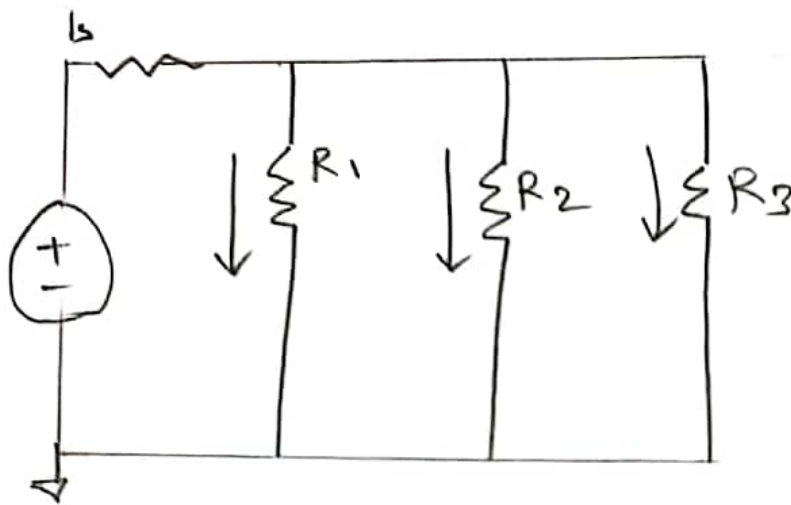

current divider formula: $I_x = \frac{I_t}{R_n} R_t$

Kirchhoff's Current Law (KCL) states that the algebraic sum of currents entering and leaving junction (or node) in an electrical circuit is 0.


In equation form, the above statement can be written as follows:

$$\sum I_i = \sum I_o$$

I_i representing current entering and I_o representing current leaving.

The combination of series and parallel circuit is called ladder circuit.


Example of a ladder circuit:

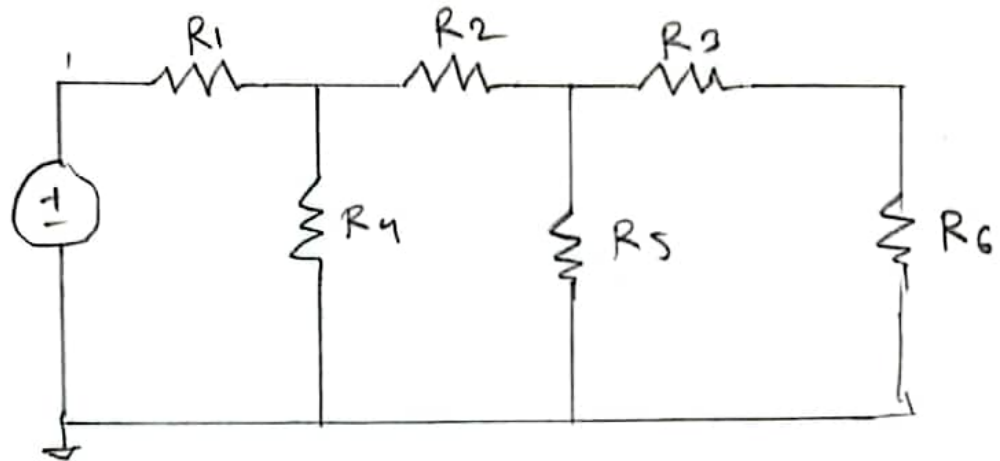


A Ladder circuit.

A color code is used to identify the values of resistors to be used in a circuit.

5. Circuit Diagrams:

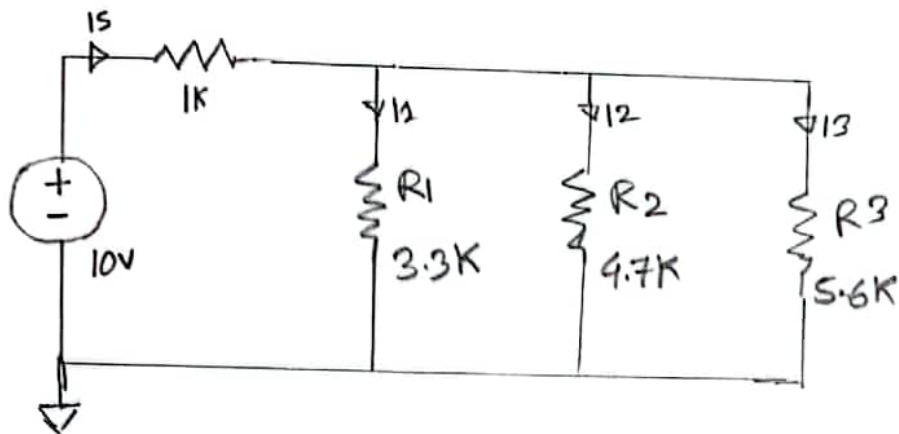

Circuit 1

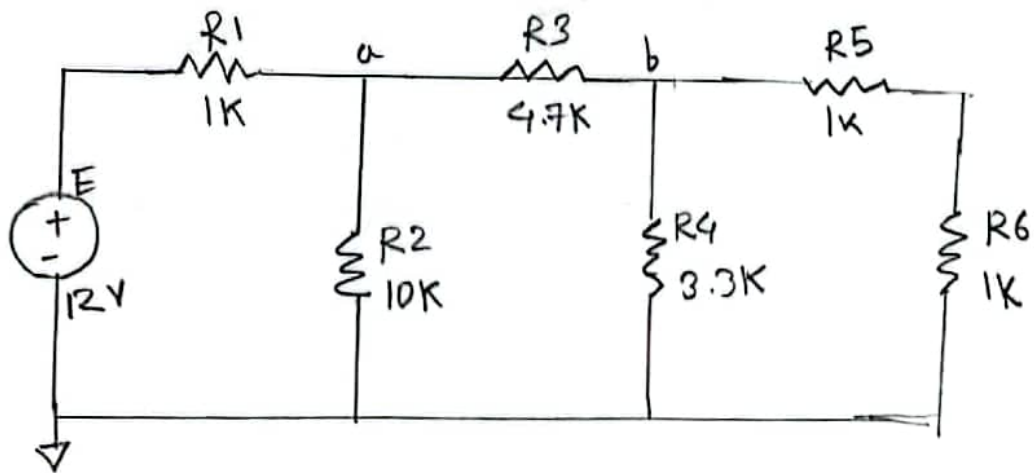

Circuit 2

Table 1:

Data Table:

Resistance using colour coding					Resistance DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance		
Brown	Black	Red	Gold	$(950 - 1050)$	0.98	2
Orange	Orange	Red	Gold	$(3135 - 3465)$	3.21	2.72
Yellow	purple	Red	Gold	$(4465 - 4935)$	4.62	1.70
Green	Blue	violet	Gold	5.32×10^8 5.88×10^8	5.61	0.17

Table 2:

Experimental readings				Theoretical values			
I_s	I_{R1}	I_{R2}	I_{R3}	I_s	I_{R1}	I_{R2}	I_{R3}
4.18	1.84	1.28	1.03	4.08	1.78	1.25	1.03
% Error							
I_s	I_{R1}	I_{R2}	I_{R3}				
2.20%	3.34%	2.4%	1.94%				

Table 3:

I_s	4.08	sum?
$(I_{R1} + I_{R2} + I_{R3})$	4.17	

Table 4:

Experimental Req	Theoretical Req	% Error
2.40	2.44	1.63%

Table 5:

Component	Voltage	Current
E	12.09	2.59
R1	2.46	2.61
R2	9.61	0.67
R3	5.82	1.64
R4	3.28	0.62
R5	0.98	1.02
R6	0.97	1.01

Discussion :

In this experiment, we used four resistors. First, we calculated their resistance using color coding and take the values. Then, we placed them on trainer board and measured their actual resistance with a digital Multimeter. The circuit was built with four resistors: $1k\Omega$, $3.3k\Omega$, $4.7k\Omega$, $5.6k\Omega$.

Then we built the circuit. We set our DMM to mA mode and connected the red wire to the Ampere. We measured the current of each resistor. Then we disconnected the circuit from the source and measured the Req.

we added the current flow through each resistor in parallel and compared it to that of the resistor in series. The values were not exactly same. the difference was negligible. we also calculate the percentage of error.

$$\% \text{ Error} = \frac{|\text{practical value} - \text{theoretical}|}{\text{Theoretical}} \times 100$$

Next we built circuit 2. we measured the voltage across each resistor by connecting the DMM in parallel. Then, we measured the current through each resistor by connecting the DMM in series. we keep the values in table 5.

we completed our lab experiment without any major issues. Minor issues were solved by our lab instructor. This lab experiment was very helpful and we got to know about how to measure voltage, current and resistance by DMM and verify KVL, KCL and calculate percentage of error.

NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



EEE41L/ETE141L

Sum of individual Current ($I_{R1} + I_{R2} + I_{R3}$)	4.17	
---	------	--

Table 4:

Experimental Req	Theoretical Req	% Error
2.40	2.49	1.63

Table 5:

Component	Voltage	Current
E	12.09	2.59
R1	2.46	2.61
R2	9.61	0.67
R3	5.82	1.64
R4	3.28	0.62
R5	0.98	1.02
R6	0.97	1.01

Report

1. State the current division rule.
2. State the Kirchhoff's current law (KCL).
3. With the experimental data, verify Kirchhoff's voltage law in Circuit 1 within each independent closed loop of the circuit.
4. With the experimental data, verify Kirchhoff's current law at nodes *a* and *b* of circuit 2.
5. Showing all steps, calculate the theoretical values in Table 2. Compare theoretical values to your experimental values and explain whether your circuit follows KCL or not.
6. Showing all the steps, theoretically calculate Req of circuit 1. Compare with the experimental value.
7. Calculate all the theoretical values for Table 5. Show all steps.

Useful Formula:

Current Divider Rule : $I_x = I_s R_T / R_x$

% Error = (Theoretical value - Experimental Value) / Theoretical Value

NORTH SOUTH UNIVERSITY

DEPARTMENT OF ELECTRICAL & COMPUTER ENGINEERING



EEE41L/ETE141L

8. Now, disconnect the voltage source from the circuit and measure the total load resistance, Req of the circuit using DMM. Note down values in Table 4.
9. Construct Circuit 2.
10. Using a DMM, measure the potential differences across all the resistors in circuit 2. Record all the readings in Table 5
11. Using a DMM, measure the current through all the resistors and record in Table 5.

Data Collection

Lab 2

Group No. _____

Instructor's Signature _____

Table 1:

Resistance using colour coding					Resistance using DMM	% Error
Band 1	Band 2	Band 3	Band 4	Resistance \pm tol		
Brown	Black	Red	Gold	(950-1050)	0.98	2
Orange	Orange	Red	Gold	(3135-3465)	3.21	2.72
Yellow	Purple	Red	Gold	(4465-4735)	4.62	1.70
Green	Blue	Violet	Gold	$5.32 \times 10^8 - 5.61 \times 10^8$	5.61	0.17

Table 2:

Experimental readings				Theoretical values			
I_S	I_{R1}	I_{R2}	I_{R3}	I_S	I_{R1}	I_{R2}	I_{R3}
4.18	1.84	1.28	1.05	4.08	1.78	1.25	1.03
% Error							
I_S	I_{R1}		I_{R2}		I_{R3}		
2.20%	3.31%		2.4%		1.94%		

Table 3:

I_S	4.08	I_S Total Current equal to sum individual current?
-------	------	--